

# CS2002 Logic Lecture 7

## Sequential Circuits

Ian Gent

# Last time

- Combinational Circuits
- Circuits for Arithmetic
  - half adders and full adders
  - n-bit ripple adders
- Circuits for other activities in computers

# This Time

- Sequential Logic Circuits
- Interlude: LogicSim for simulating circuits

# Combinational vs Sequential Circuits

# Combinational vs Sequential Circuits

## Combinational Circuits

- Everything we've seen so far
- Data flows from input to output
- Outputs are fully determined by **current** inputs
- After stabilisation
  - All you need to know is the corresponding **truth table**

# Combinational vs Sequential Circuits

## Combinational Circuits

- Everything we've seen so far
- Data flows from input to output
- Outputs are fully determined by **current** inputs
- After stabilisation
  - All you need to know is the corresponding **truth table**


## Sequential Circuits

- May have feedback loops
- Circuit has **state**
  - future behaviour determined by **past** state and current inputs
- more complex to model
- needed to make interesting computers

# Feedback in Circuits

- Let's see a simple example of feedback
- Feeding back the output of gates to their input
- What happens?

# Feedback Example

 



# What Happens? (1)

Set  $R=0$ ,  $S=0$

$Q=Q'=1$

$Q$  and  $Q'$  feedback to NANDs

Now set  $R=1$


$Q = 1 \text{ NAND } 1 = 0$

$Q' = 0 \text{ NAND } 0 = 1$

Now set  $S = 1$

Nothing changes

Result:  $R=S=1$ ,  $Q=0$ ,  $Q'=1$

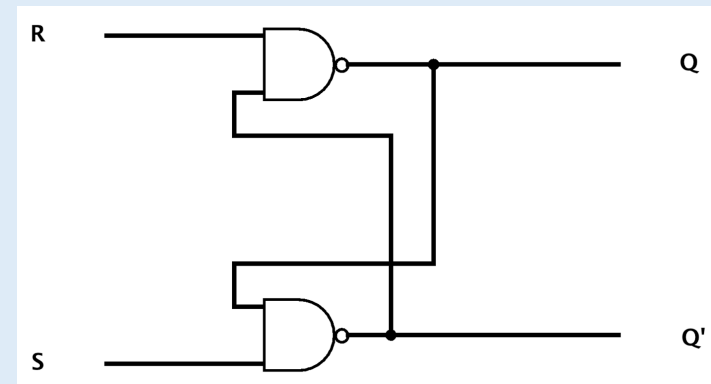

# What Happens? (2)

Set  $R=0$ ,  $S=0$

$Q=Q'=1$

$Q$  and  $Q'$  feedback to NANDs

Now set  $S=1$


$Q' = 1 \text{ NAND } 1 = 0$

$Q = 0 \text{ NAND } 0 = 1$

Now set  $R=1$

Nothing changes

Result:  $R=S=1$ ,  $Q=1$ ,  $Q'=0$

 


# What Happened?

If we set  $R=1$  first then  $S=1$  we get  
Result:  $R=S=1, Q=0, Q'=1$


If we set  $S=1$  first then  $R=1$  we get  
Result:  $R=S=1, Q=1, Q'=0$

For the same inputs the result  
depends on the sequence of inputs  
over time


This is a sequential circuit

 

# What Can Happen?

 

# What Can Happen?

 


Note:  
This assumes something

*R, S not allowed to  
Change simultaneously*


# RS NAND Latch

| R | S | Q | Q' |
|---|---|---|----|
| 0 | 0 | 1 | 1  |
| 0 | 1 | 1 | 0  |
| 1 | 0 | 0 | 1  |
| 1 | 1 | ? | ?  |

 


- ?s Depend on whether R or S got to 1 first
- Unstable if we switch R and S from 0 to 1 together
- Stable with  $Q = 0, Q' = 1$  or vice versa

# Memory Example: Unclocked D Latch

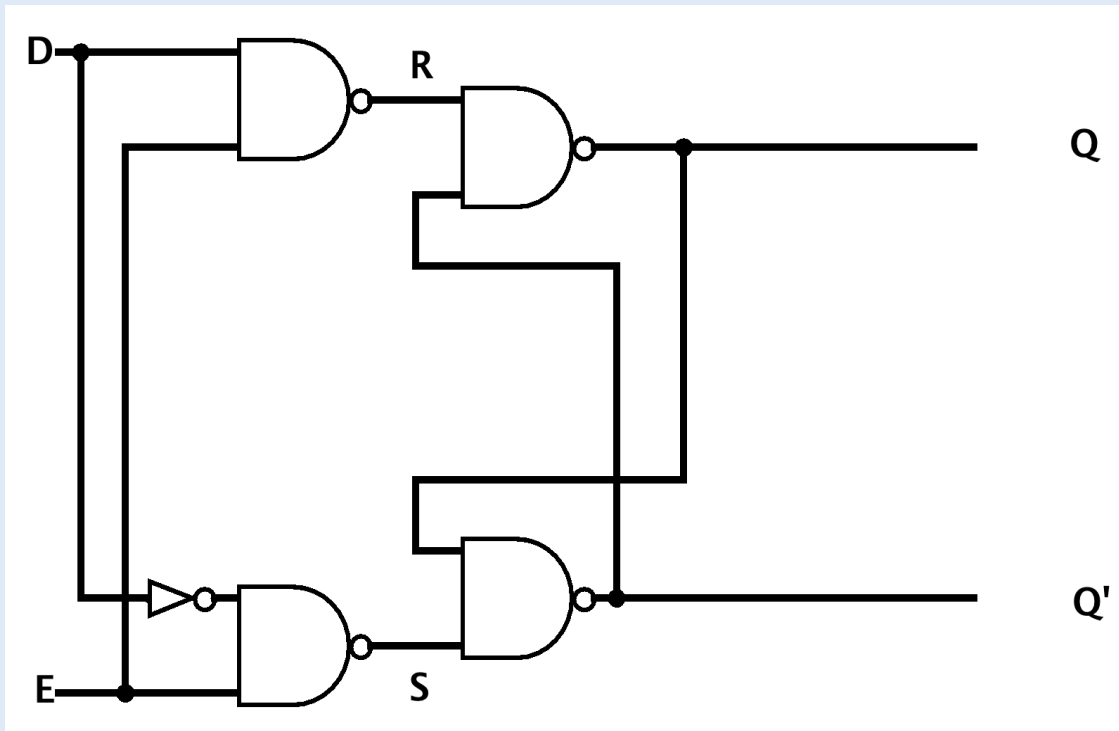

- Called an (unclocked) D latch
- We have conditioning logic on the left
- Feeds into RS NAND Latch on Right
- E stands for “Enable”
- But what does E enable?


# Memory Example: Unclocked D Latch

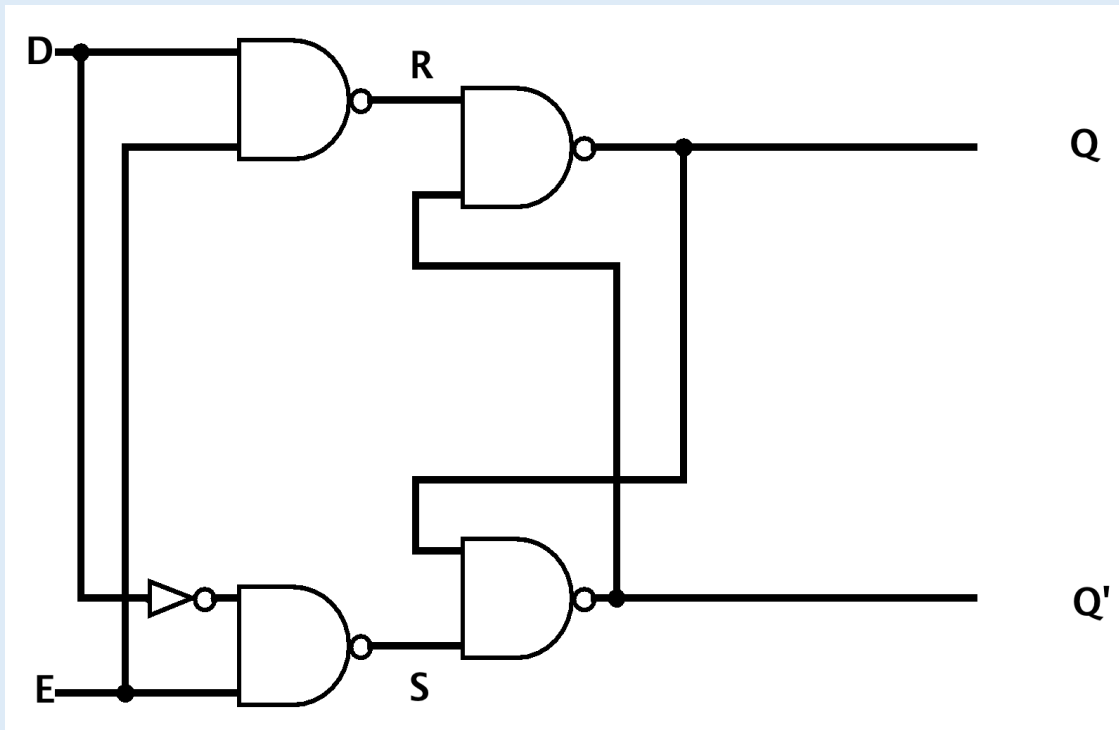

- But what does E enable?
- $E = 0$ 
  - $R = S = 1$
  - Q fixed
  - D ignored
- $E = 1$ 
  - $R = \neg D, S = D$
  - $Q = S = D$
- R and S never both 0
- Note that unlike raw RS NAND Latch, no state is undefined




# Memory Example: Unclocked D Latch

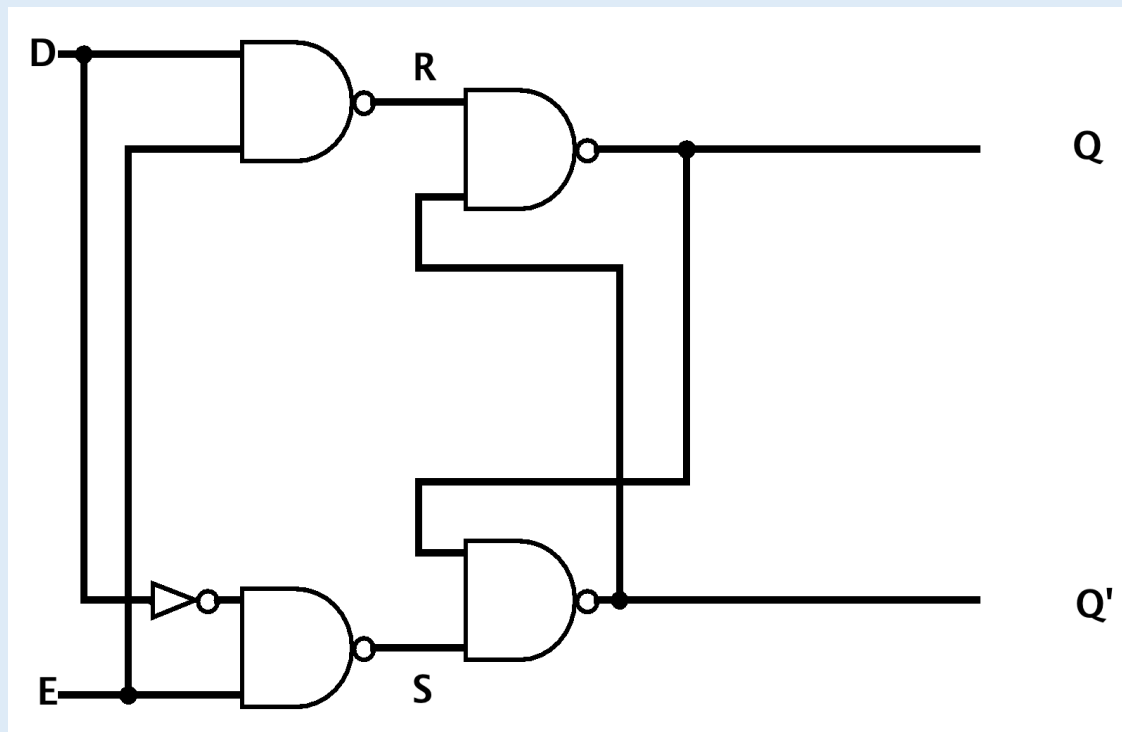

- **E** is write-Enable
- **D** is Data
- Output is value of D last time E was 1
- Basic bit of memory

# Interlude: LogicSim

# Interlude: LogicSim

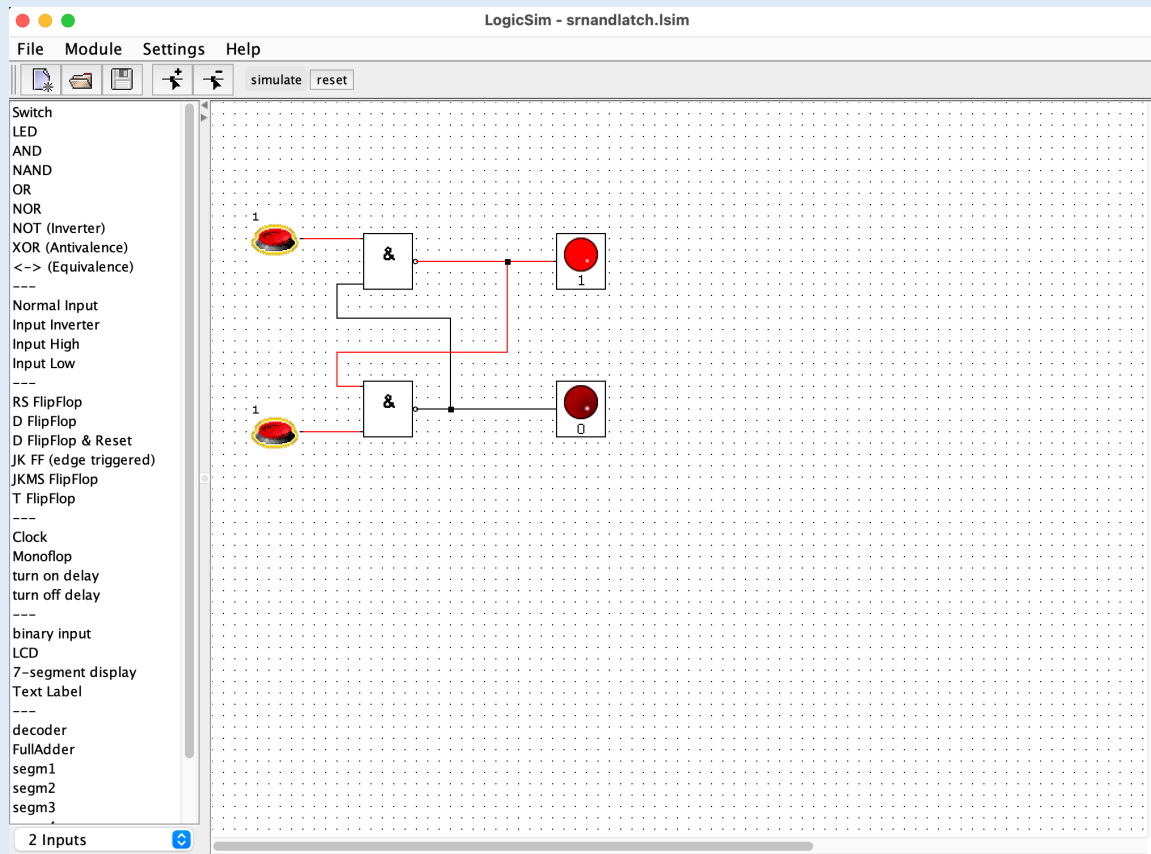

Useful tool for exploring circuit Behaviour

Runs from java


Available on Studres  
under "Exercises"

Video by Mark-Jan Nederhof  
Gives you a quick guide

Feel free to use other logic  
simulators
 
# A Clock Signal

- The clock signal changes regularly from 0 to 1 and back again
- Clock cycle is time to go from 0 to 1 and back again



**Rising edges  
of the clock**

**Falling edges  
of the clock**


**Clock Cycle  
Time**

**Clock signal**

# CPU Clocks


- CPU has a clock signal distributed to all parts of it
  - care needed to keep it in sync
  - also consumes a lot of power
- State of CPU is defined by design on edges of the clock only
  - each state follows logically from the one before
  - latches etc. are used to make this work
  - clock cycle has to be long enough to allow for all gate delays
- 1951 Ferranti Mark 1 - 1.2ms (milliseconds)
- 1976 Cray 1 - clock cycle 12.5ns, Z80 400ns (nanoseconds)
- 2005 Pentium IV, clock cycle 260ps (picoseconds)
- 2021 AMD's, Ryzen TR 3990X clock cycle (in boost mode) **232ps**
  - Note lack of speedup in 15 years though the TR3990X has 64 cores!

# Clocked Example

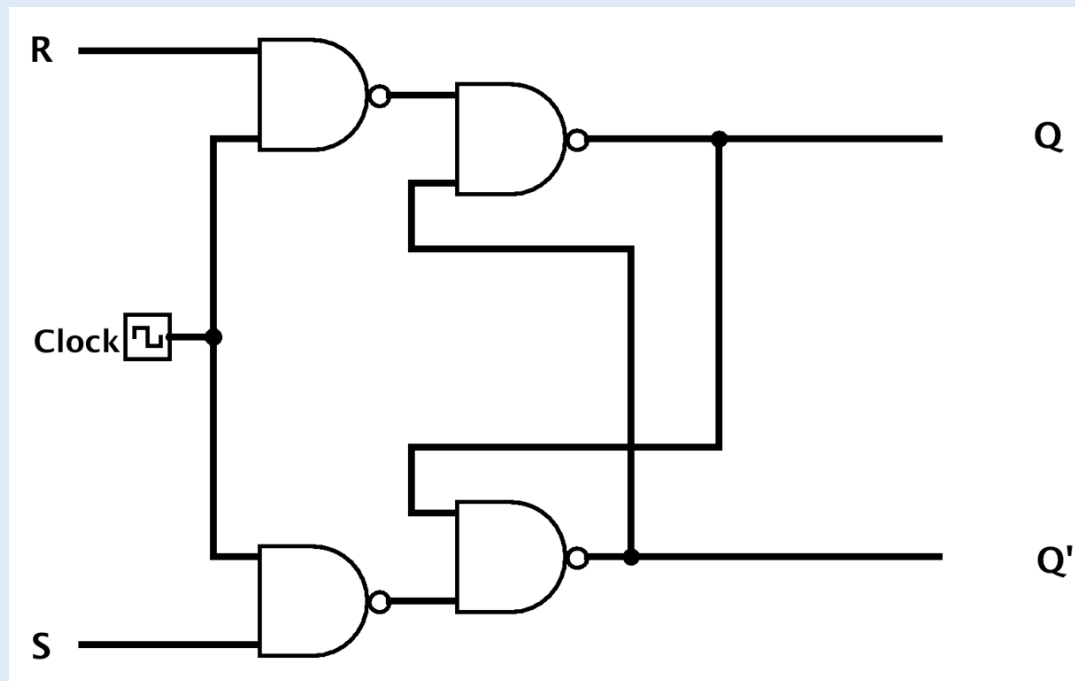
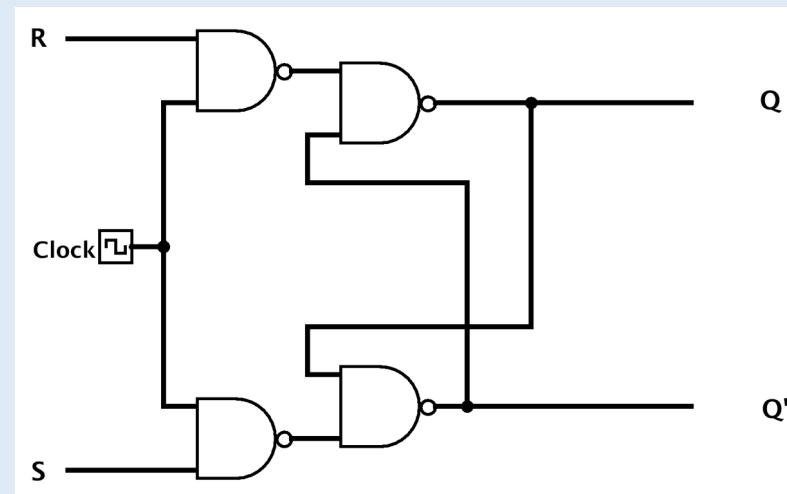
# Clocked RS NAND Latch

- RS NAND Latch guarded by NANDS and clock
- When Clock is 0 output of first NANDS must be 1
  - Q and Q' will not change
  - A simple form of memory
- When clock goes to 1
  - R and S can change Q/Q'



# Multistage computation example

| Cycle | Clock value | Stage | Type          | Notes                                                       |
|-------|-------------|-------|---------------|-------------------------------------------------------------|
| 17    | 1           | 1     | Combinational |                                                             |
| 17    | 1           | 2     | Latch         |                                                             |
| 17    | 0           | 3     | Combinational | stage 3 runs using stabilized results from stage 1          |
| 17    | 0           | 4     | Latch         |                                                             |
| 18    | 1           | 1     | Combinational | stage 1 runs may use results from stage 4 of previous cycle |
| 18    | 1           | 2     | Latch         |                                                             |



# Basic Concepts of Sequential Circuits

- A sequential circuit defines its output in terms of both its current inputs and its previous inputs
- To remember previous inputs, we need a storage element – e.g. flip-flop, latch
- The state of the latch is a function of the previous inputs to the circuit
- We need event ordering
- **Synchronous** sequential circuits use clocks to order events - activities synchronise with clock signals
- We pretend time is discrete: hence the notion of a clock “tick”

# Next Time

- Flip Flops